

Arduino Air Piano Project

Objective: Build a basic air piano that plays different tones based on hand distance, lighting up LEDs for visual feedback. The ultrasonic sensor detects hand distance, triggering different tones and LEDs.

Components

- **Arduino Uno** - 1
- **Breadboard** - 1
- **Jumper Wires** - Assorted
- **LEDs:**
 - Red LED - 1
 - Yellow LED - 1
 - Green LED - 1
- **Resistors:**
 - 220Ω resistor (for each LED) - 3
- **Buzzer or Speaker** - 1
- **Button** - 1
- **Ultrasonic Sensor** - 1 (e.g., HC-SR04)

Wiring Diagram and Setup

1. **Connect the LEDs:**
 - **Red LED:**
 - Connect the **positive (longer) leg** to digital pin 8 on the Arduino through a 220Ω resistor.
 - Connect the **negative leg** to the **ground (GND)** on the breadboard.
 - **Yellow LED:**
 - Connect the **positive leg** to digital pin 9 through a 220Ω resistor.
 - Connect the **negative leg** to GND on the breadboard.
 - **Green LED:**
 - Connect the **positive leg** to digital pin 10 through a 220Ω resistor.
 - Connect the **negative leg** to GND on the breadboard.
2. **Connect the Buzzer/Speaker:**
 - Connect the **positive pin** of the buzzer to digital pin 8.
 - Connect the **negative pin** to GND.
3. **Connect the Ultrasonic Sensor (HC-SR04):**

- Connect the **VCC** pin to the 5V pin on the Arduino.
 - Connect the **GND** pin to GND on the Arduino.
 - Connect the **Trig** pin to digital pin 13.
 - Connect the **Echo** pin to digital pin 12.
4. **Connect the Button:**
- Connect one of the pins of the button to digital pin 6.
 - Connect the other pin to GND.
5. **Download the code posted to the git and upload it to the Arduino.**

Once you complete these steps, you are good to go!